

AEC Test4

20001003100@jcbosust.ac.in [Switch account](#)



Your email will be recorded when you submit this form


The input to the differentiator circuit is a sinusoidal voltage of peak value 8mV and frequency 1kHz. Find the output voltage if $R = 100\text{k}\Omega$ and $C = 1\mu\text{F}$ 1 point

- ☐ $-\pi\cos(2000\pi t)$ Volts
- ☐ $-2\pi\cos(1000\pi t)$ Volts
- ☐ $-0.8\pi\sin(2000\pi t)$ Volts
- ☐ $-1.6\pi\cos(2000\pi t)$ Volts

The differential voltage gain and CMRR of an opamp when expressed in dB 1 point
are 110dB and 100dB respectively. Determine the common mode gain.


- ☐ 24dB
- ☐ 10dB
- ☐ 6.5dB
- ☐ 20dB

For the given circuit find V_o . 1 point

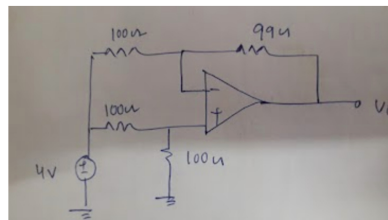


- ☐ 0.02V
- ☐ 0.2V
- ☐ 2V
- ☐ 0.04V

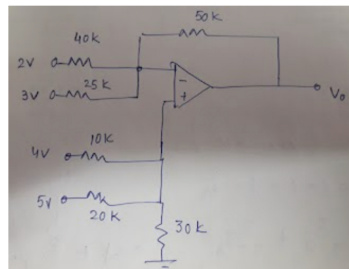
Find the output voltage of the given circuit. 1 point



- ☐ 4V
- ☐ 6.568V
- ☐ 12.656V
- ☐ 16.765V

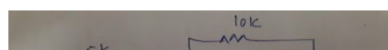Find the output voltage of the given circuit. 1 point




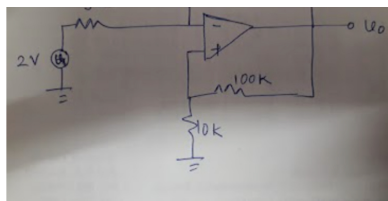

- ☐ -5.5V
- ☐ -6.5V
- ☐ 6.5V
- ☐ 5.5V


For the given circuit find V_o .

1 point

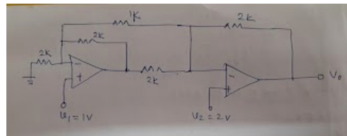

- ☐ 5V
- ☐ 2V
- ☐ 6V
- ☐ 4V

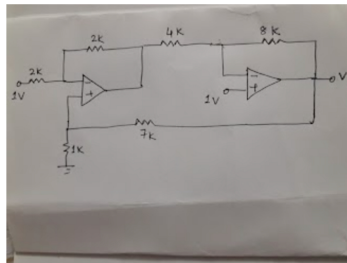
Find the output voltage of the following circuit shown below, assume ideal opamp. 1 point



- ☐ $8/3$ V
- ☐ 4V
- ☐ $10/3$ V
- ☐ $4/3$ V

Find the expression of output voltage $V_o(S)$.


1 point

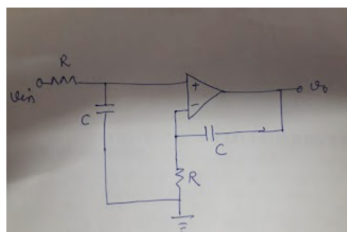

- ☐ $(1/RCS) \cdot V_{in}(S)$
- ☐ $-RCS V_{in}(S)$
- ☐ $RCS V_{in}(S)$
- ☐ $-(1/RCS) \cdot V_{in}(S)$

Find the expression of output voltage $V_o(S)$.

1 point

Captionless Image

- ☐ $(1/RCS)*V_{in}(S)$
- ☐ $2RCSV_{in}(S)$
- ☐ $(2/RCS)*V_{in}(S)$
- ☐ $-2RCSV_{in}(S)$

A triangular wave input of 6V peak to peak magnitude and frequency of 2MHz is applied to a voltage follower. What is the slew rate of the opamp.

1 point

- ☐ $20V/\mu s$
- ☐ $30V/\mu s$
- ☐ $24V/\mu s$
- ☐ $34V/\mu s$

Submit

Clear form

This form was created inside of JC Bose University of Science and Technology, YMCA Faridabad. [Report Abuse](#)

Google Forms